

Keywords: voltage regulation, op amps, pnp transistors, linear regulators

APPLICATION NOTE 4405

# Spare Op Amp Generates Its Own Regulated Negative Supply

Jun 05, 2009

*Abstract: This application note shows how to use a spare op amp to generate a regulated negative voltage supply, used to power the op amp itself as well as other low current circuitry. The regulated negative supply is generated from a regulated positive voltage and an unregulated negative voltage.*

This design idea appeared in the April 14, 2006 issue of *EE Times*.

For systems that require low current (100mA or less) and include a spare op amp along with unregulated positive and negative voltages, the circuit of **Figure 1** generates a regulated positive and negative supply voltage. The op amp then operates from the supply rails that it has helped to generate ( $\pm 5V$  in this case). **Figure 2** shows the power-up response. The circuit achieves regulation regardless of which unregulated voltage is applied first.

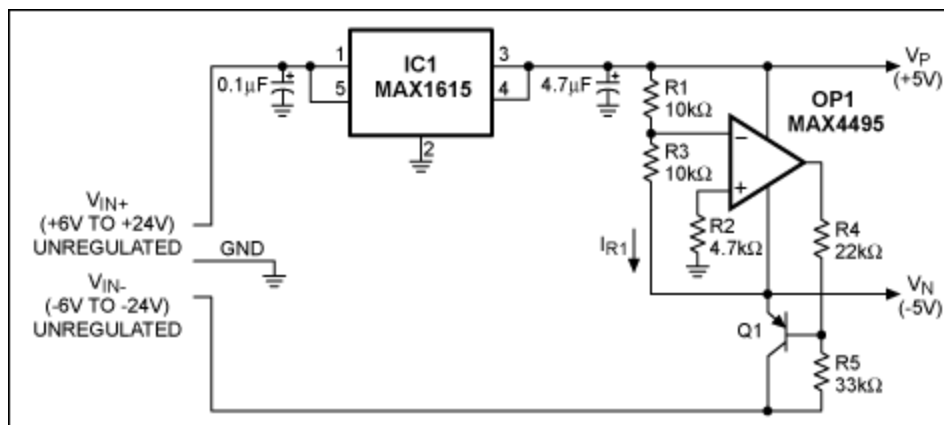


Figure 1. This circuit derives a regulated  $\pm$  voltage from  $\pm$  unregulated input voltages.

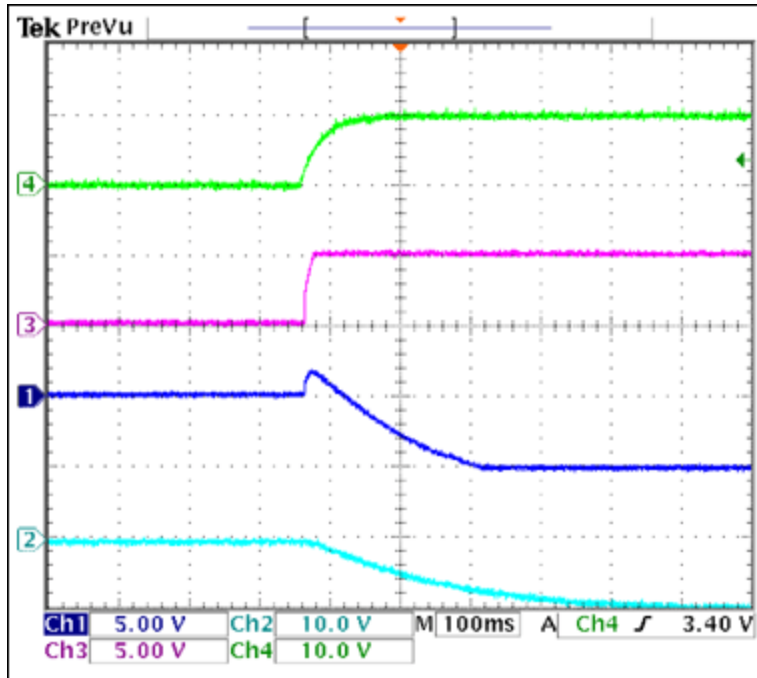


Figure 2. The power-up response for the Figure 1 circuit.

CH1 = regulated -5V output  
 CH2 = negative supply voltage  
 CH3 = regulated +5V output  
 CH4 = positive supply voltage

By controlling the base drive to Q1, the op amp maintains equilibrium at its inverting input, and thereby ensures that  $V_N = -V_P(R3/R1)$ . Resistor R5 provides the initial base current to Q1 until OP1 takes over. When that happens, OP1, Q1, and R1, R3, R4, and R5 form a negative feedback network that regulates  $V_N$  to  $-V_P(R3/R1)$ :

$$V_{OP1+} = V_{OP1-}$$

$$V_{OP1+} = 0V$$

Using Superposition:

$$V_{OP1-' } = V_P(R3/(R3+R1))$$

$$V_{OP1-''} = (V_N(R1/(R1+R3)))$$

$$V_{OP1-} = V_{OP1-' } + V_{OP1-''}$$

$$V_{OP1-} = V_P(R3/(R3+R1)) + V_N(R1/(R1+R3))$$

$$V_N = -V_P(R3/(R3+R1))((R1+R3)/R1)$$

Therefore:

$$V_N = -V_P(R3/R1)$$

Alternatively:

$$I_{R1} = V_P/R1$$

Therefore:

$$V_N = -I_{R1} \times R3 = (-V_P/R1)R3$$

The allowable range of the unregulated negative supply voltage is -6V to -24V. For a wider input-supply range, either replace Q1 with a higher gain transistor or lower the resistance of R4 and R5.  $V_N$  can deliver up to 100mA without distortion, but  $V_P$  is limited by the reference of IC1 to a maximum of 30mA, with a  $V_P$  reduction at that level of ~0.3V. (For higher positive load currents you can substitute a different positive regulator.)

$I_{BIAS}$  is negligible for the op amp shown. To minimize the  $I_{BIAS}$  error for other op amps, R2 should have the value  $R1||R3$ .

#### Related Parts

[MAX1615](#)

High-Voltage, Low-Power Linear Regulators for Notebook Computers

[Free Samples](#)

---

#### More Information

For Technical Support: <http://www.maximintegrated.com/support>

For Samples: <http://www.maximintegrated.com/samples>

Other Questions and Comments: <http://www.maximintegrated.com/contact>

---

Application Note 4405: <http://www.maximintegrated.com/an4405>

APPLICATION NOTE 4405, AN4405, AN 4405, APP4405, Appnote4405, Appnote 4405

Copyright © by Maxim Integrated Products

Additional Legal Notices: <http://www.maximintegrated.com/legal>